

Circuit Design and Simulation with VHDL

2nd edition

Volnei A. Pedroni

MIT Press, 2010

Book web: www.vhdl.us

Solutions Manual (v4)

VHDL

Exercises covered

Chapter 1: Introduction	---
Chapter 2: Code Structure	1
Chapter 3: Data Types	1, 9, 15, 20, 23, 30
Chapter 4: Operators and Attributes	4, 6, 8, 9, 13
Chapter 5: Concurrent Code	4, 7, 11, 20
Chapter 6: Sequential Code	1, 4, 8, 9, 12, 13
Chapter 7: SIGNAL and VARIABLE	3, 4, 7, 9
Chapter 8: PACKAGE and COMPONENT	6, 8
Chapter 9: FUNCTION and PROCEDURE	1, 5, 6
Chapter 10: Simulation with VHDL Testbenches	1, 11, 12

Extended and Advanced Designs

Exercises covered

Chapter 11: VHDL Design of State Machines	4, 6, 11, 15
Chapter 12: VHDL Design with Basic Displays	2, 13
Chapter 13: VHDL Design of Memory Circuits	5, 9
Chapter 14: VHDL Design of Serial Communications Circuits	10
Chapter 15: VHDL Design of VGA Video Interfaces	1, 2, 3, 4, 6
Chapter 16: VHDL Design of DVI Video Interfaces	2, 3, 4, 6
Chapter 17: VHDL Design of FPD-Link Video Interfaces	2, 3, 4

Exercise 2.1: Multiplexer

a) Code

```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY mux IS
6      PORT (
7          a, b: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
8          sel: IN STD_LOGIC_VECTOR(1 DOWNTO 0));
9          x: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
10 END mux; --or END ENTITY;
11 -----
12 ARCHITECTURE example OF mux IS
13 BEGIN
14     PROCESS (a, b, sel)
15     BEGIN
16         IF (sel="00") THEN
17             x <= "00000000";
18         ELSIF (sel="01") THEN
19             x <= a;
20         ELSIF (sel="10") THEN
21             x <= b;
22         ELSE
23             x <= "ZZZZZZZZ";
24         END IF;
25     END PROCESS;
26 END example; --or END ARCHITECTURE;
27 -----
28 -----

```

b) Comments:

Lines 2–3: Library/package declarations. Because the type `STD_LOGIC` is employed, the package `std_logic_1164` must be included. The other two indispensable libraries (`std` and `work`) are made visible by default.

Lines 5–10: ENTITY, here named *mux*.

Lines 7-9: Specifications of all input and output ports (all of type `STD_LOGIC_VECTOR` in this example).

Lines 12–27: ARCHITECTURE, here named *example*.

Lines 14–26: A PROCESS was employed to construct the circuit. Its sensitivity list (line 13) contains the signals *a*, *b*, and *sel*, so whenever one of these signals changes its value the process is run.

Lines 16-25: In the process, the IF statement was used to implement the multiplexer, according to the truth table of figure 2.9.

Lines 1, 4, 11, 28: Used just to improve code readability (these lines separate the three fundamental code sections).

Exercise 3.1: Possible data types #1

```

s1 <= '0';           --BIT, STD_LOGIC, CHARACTER
s2 <= 'Z';           --STD_LOGIC, CHARACTER
s3 <= TRUE;          --BOOLEAN
s4 <= "01000";       --BIT_VECTOR, STD_LOGIC_VECTOR, SIGNED, UNSIGNED, STRING
Note: Above, STD_LOGIC means STD_LOGIC and STD_ULOGIC

```

Exercise 3.9: Possible packages

a) None, because arithmetic and comparison operators for INTEGER are already included in the definition package (*standard*), which is visible by default.

b) Either *std_logic_unsigned* or *std_logic_signed*. If VHDL 2008 has already been implemented, *numeric_std_unsigned* is another option.

Exercise 3.15: 1Dx1D array examples

```

TYPE type1 IS ARRAY (NATURAL RANGE <>) OF BIT_VECTOR(7 DOWNTO 0);
TYPE type2 IS ARRAY (1 TO M) OF BIT_VECTOR(N-1 DOWNTO 0);
TYPE type3 IS ARRAY (1 TO M) OF NATURAL RANGE 0 TO 2**N-1;

```

Exercise 3.20: Type conversion by specific functions

Figure 3.10 is very helpful to solve this exercise. Type casting was also included in some cases (see figure 3.10 of the book).

- a) INTEGER to SLV: Function *conv_std_logic_vector(a, cs)*, from the package *std_logic_arith*.
- b) BV to SLV: Function *to_stdlogicvector(a, cs)*, from the package *std_logic_1164*.
- c) SLV to UNSIGNED: Function *unsigned(a)*, from the package *numeric_std* or *std_logic_arith*.
- d) SLV to INTEGER: Function *conv_integer(a, cs)*, from the package *std_logic_signed* or *std_logic_unsigned*, or function *to_integer(a, cs)*, from *numeric_std_unsigned*.
- e) SIGNED to SLV: Function *std_logic_vector(a)*, from the package *numeric_std* or *std_logic_arith*, or function *conv_std_logic_vector(a, cs)* from *std_logic_arith*.

Exercise 3.23: Array dimensionality

```
SIGNAL s1: BIT;                                --scalar (a single bit)
SIGNAL s2: BIT_VECTOR(7 DOWNT0 0);             --1D (a vector of bits)
SIGNAL s3: STD_LOGIC;                          --scalar (single bit)
SIGNAL s4: STD_LOGIC_VECTOR(7 DOWNT0 0);       --1D (vector of bits)
SIGNAL s5: INTEGER RANGE -35 TO 35;            --1D (vector of bits)
VARIABLE v1: BIT_VECTOR(7 DOWNT0 0);          --1D (vector of bits)
VARIABLE v2: INTEGER RANGE -35 TO 35;         --1D (vector of bits)
```

Exercise 3.30: Illegal assignments #3

- a) `s4(0)(0) <= s7(1,1,1);` --cause 1 (BIT x STD_LOGIC)
- b) `s6(1) <= s4(1);` --cause 2 (pile of BIT_VECTOR x single BIT_VECTOR)
- c) `s1 <= "00000000";` --cause 3 (individual values must be TRUE or FALSE)
- d) `s7(0)(0)(0) <= 'Z';` --cause 4 (zero is invalid index) + cause 3 (wrong parenthesis)
- e) `s2(7 DOWNT0 5) <= s1(2 DOWNT0 0);` --cause 1 (slice with BIT x slice with BOOLEAN)
- f) `s4(1) <= (OTHERS => 'Z');` --cause 3 ('Z' is an invalid value for BIT)
- g) `s6(1,1) <= s2;` --cause 4 (the correct index is s6(1)(1))
- h) `s2 <= s3(1) AND s4(1);` --invalid AND operator (for INT.) + cause 1 (type2 x INTEGER x BV)
- i) `s1(0 TO 1) <= (FALSE, FALSE);` --cause 4 (index of s1 must be downward)
- j) `s3(1) <= (3, 35, -8, 97);` --cause 2 (single INTEGER x pile of INTEGER)

Exercise 4.4: Logical operators

- a) `a(7 DOWNT0 4) NAND "0111" → "1100"`
- b) `a(7 DOWNT0 4) XOR NOT b → "1100"`
- c) `"1111" NOR b → "0000" → "0000"`
- d) `b(2 DOWNT0 0) XNOR "101" → "101"`

Exercise 4.6: Arithmetic operators #2

- a) $x \text{ REM } y = 65 \text{ REM } 7 = 65 - (65/7)*7 = 2$
- b) $x \text{ REM } -y = 65 \text{ REM } -7 = 65 - (65/-7)*-7 = 2$
- c) $(x + 2*y) \text{ REM } y = 79 \text{ REM } 7 = 79 - (79/7)*7 = 2$
- d) $(x + y) \text{ REM } -x = 72 \text{ REM } -7 = 72 - (72/-65)*-65 = 7$
- e) $x \text{ MOD } y = 65 \text{ MOD } 7 = 65 \text{ REM } 7 + 0 = 2$
- f) $x \text{ MOD } -y = 65 \text{ MOD } -7 = (65 \text{ REM } -7) + (-7) = 2 - 7 = -5$
- g) $-x \text{ MOD } -y = -65 \text{ MOD } -7 = (-65 \text{ REM } -7) + 0 = -65 - (-65/-7)*-7 = -2$
- h) $\text{ABS}(-y) = \text{ABS}(-7) = 7$

Exercise 4.8: Shift and concatenation operators

- | | |
|-------------------------------------|--|
| a) <code>x SLL 3 = "010000"</code> | a) <code>x(2 DOWNTO 0) & "000";</code> |
| b) <code>x SLA -2 = "111100"</code> | b) <code>x(5) & x(5) & x(5 DOWNTO 2);</code> |
| c) <code>x SRA 2 = "111100"</code> | c) <code>x(5) & x(5) & x(5 DOWNTO 2);</code> |
| d) <code>x ROL 1 = "100101"</code> | d) <code>x(4 DOWNTO 0) & x(5);</code> |
| e) <code>x ROR -3 = "010110"</code> | e) <code>x(2 DOWNTO 0) & x(5 DOWNTO 3);</code> |

Exercise 4.9: Arithmetic operators for signed types

- | | |
|--|--|
| a) <code>x <= a + b;</code> | --either numeric_std or std_logic_arith is fine (see note 1) |
| b) <code>x <= b + c;</code> | --either numeric_std or std_logic_arith is fine (see note 1) |
| c) <code>x <= 3*b;</code> | --only numeric_std is fine (see note 2) |
| d) <code>x <= 3*a + b;</code> | --only numeric_std is fine (see note 3) |
| e) <code>x <= a + c + "1111";</code> | --only numeric_std is fine (see notes 1 and 4) |
| f) <code>x <= a + c + SIGNED'("1111");</code> | --either numeric_std or std_logic_arith is fine (see note 5) |

Notes:

- 1) Output size (number of bits) must be equal to the largest input
- 2) Output size must be twice the input size
- 3) Output size must be equal to the sum of the two input sizes
- 4) Note that "1111" is signed, determined by context
- 5) Note the use of a qualified expression (see section 3.17)

Exercise 4.13: The *enum_encoding* attribute

- a) Sequential: $a="000", b="001", c="010", d="011", e="100", f="101"$
 b) Gray: $a="000", b="001", c="011", d="010", e="110", f="111"$
 c) Johnson: $a="000", b="100", c="110", d="111", e="011", f="001"$
 or $a="000", b="001", c="011", d="111", e="110", f="100"$
 d) One-hot: $a="000001", b="000010", c="000100", d="001000", e="010000", f="100000"$

Exercise 5.4: Generic parity generator

Note in the code below the use of the recommendation introduced in section 7.7.

```

1  -----
2  ENTITY parity_generator IS
3      GENERIC (N: INTEGER := 8); --number of bits
4  PORT (
5      x: IN BIT_VECTOR(N-1 DOWNTO 0);
6      y: OUT BIT_VECTOR(N DOWNTO 0));
7  END ENTITY;
8  -----
9  ARCHITECTURE structural OF parity_generator IS
10     SIGNAL internal: BIT_VECTOR(N-1 DOWNTO 0);
11 BEGIN
12     internal(0) <= x(0);
13     gen: FOR i IN 1 TO N-1 GENERATE
14         internal(i) <= internal(i-1) XOR x(i);
15     END GENERATE;
16     y <= internal(N-1) & x;
17 END structural;
18 -----

```

Exercise 5.7: Hamming weight with GENERATE

Note in the code below again the use of the recommendation introduced in section 7.7.

```

1  -----
2  ENTITY hamming_weigth IS
3      GENERIC (
4          N: INTEGER := 8); --number of bits
5      PORT (
6          x: IN BIT_VECTOR(N-1 DOWNT0 0);
7          y: OUT NATURAL RANGE 0 TO N);
8  END ENTITY;
9  -----
10 ARCHITECTURE hamming_weigth OF hamming_weigth IS
11     TYPE natural_array IS ARRAY (0 TO N) OF NATURAL RANGE 0 TO N;
12     SIGNAL internal: natural_array;
13 BEGIN
14     internal(0) <= 0;
15     gen: FOR i IN 1 TO N GENERATE
16         internal(i) <= internal(i-1) + 1 WHEN x(i-1)='1' ELSE internal(i-1);
17     END GENERATE;
18     y <= internal(N);
19 END ARCHITECTURE;
20 -----

```

Exercise 5.11: Arithmetic circuit with STD_LOGIC

Note in the solution below the use of the sign-extension recommendation seen in sections 3.18 and 5.7.

```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE ieee.numeric_std.all;
5  -----
6  ENTITY adder IS
7      GENERIC (
8          N: NATURAL := 4); --number of bits
9      PORT (
10         a, b: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
11         cin: IN STD_LOGIC;
12         opcode: IN STD_LOGIC_VECTOR(2 DOWNT0 0);
13         y: OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0);
14         cout: OUT STD_LOGIC);
15 END ENTITY;
16 -----
17 ARCHITECTURE adder OF adder IS
18     --define internal unsigned signals:
19     SIGNAL a_unsig, b_unsig: UNSIGNED(N-1 DOWNT0 0);
20     SIGNAL y_unsig: UNSIGNED(N DOWNT0 0);
21     --define internal signed signals:
22     SIGNAL a_sig, b_sig: SIGNED(N-1 DOWNT0 0);
23     SIGNAL y_sig: SIGNED(N DOWNT0 0);
24 BEGIN
25     --convert inputs to unsigned:
26     a_unsig <= unsigned(a);
27     b_unsig <= unsigned(b);
28     --convert inputs to signed:
29     a_sig <= signed(a);
30     b_sig <= signed(b);
31     --implement circuit and convert to std_logic:
32     WITH opcode(1 DOWNT0 0) SELECT
33         y_unsig <= ('0' & a_unsig) + ('0' & b_unsig) WHEN "00",
34                 ('0' & a_unsig) - ('0' & b_unsig) WHEN "01",
35                 ('0' & b_unsig) - ('0' & a_unsig) WHEN "10",
36                 ('0' & a_unsig) + ('0' & b_unsig) + ('0' & cin) WHEN OTHERS;
37     WITH opcode(1 DOWNT0 0) SELECT
38         y_sig <= (a_sig(N-1) & a_sig) + (b_sig(N-1) & b_sig) WHEN "00",
39                 (a_sig(N-1) & a_sig) - (b_sig(N-1) & b_sig) WHEN "01",
40                 - (a_sig(N-1) & a_sig) + (b_sig(N-1) & b_sig) WHEN "10",
41                 (a_sig(N-1) & a_sig) + (b_sig(N-1) & b_sig) + ('0' & cin) WHEN OTHERS;
42     WITH opcode(2) SELECT
43         y <= std_logic_vector(y_unsig(N-1 DOWNT0 0)) WHEN '0',
44             std_logic_vector(y_sig(N-1 DOWNT0 0)) WHEN OTHERS;
45     WITH opcode(2) SELECT
46         cout <= std_logic(y_unsig(N)) WHEN '0',
47                 std_logic(y_sig(N)) WHEN OTHERS;
48 END ARCHITECTURE;
49 -----

```

Exercise 5.20: Generic Multiplexer

a) Solution with a user-defined 2D type:

In this solution, a PACKAGE, called *my_data_types*, is employed to define a new data type, called *matrix*, which is then used in the ENTITY of the main code to specify the multiplexer's inputs.

```

1  ---Package:-----
2  PACKAGE my_data_types IS
3      TYPE matrix IS ARRAY (NATURAL RANGE <>, NATURAL RANGE <>) OF BIT;
4  END PACKAGE my_data_types;
5  -----

1  ---Main code:-----
2  USE work.my_data_types.all;
3  -----
4  ENTITY generic_mux IS
5      GENERIC (
6          M: POSITIVE := 8;    --number of inputs
7          N: POSITIVE := 4);   --size of each input
8      PORT (
9          x: IN MATRIX (0 TO M-1, N-1 DOWNT0 0);
10         sel: IN INTEGER RANGE 0 TO M-1;
11         y: OUT BIT_VECTOR (N-1 DOWNT0 0));
12  END ENTITY;
13  -----
14  ARCHITECTURE arch1 OF generic_mux IS
15  BEGIN
16      gen: FOR i IN N-1 DOWNT0 0 GENERATE
17          y(i) <= x(sel, i);
18      END GENERATE gen;
19  END ARCHITECTURE;
20  -----

```

b) Solution with a predefined type:

In this solution, no package was employed. Notice, however, that *x* was not defined as a 1Dx1D or 2D structure; instead, it was specified simply as a long vector of length $M \times N$. Though this will not affect the result, such a “linearization” might be confusing sometimes, so it is usually not recommended.


```

1  -----
2  ENTITY generic_mux IS
3      GENERIC (
4          M: POSITIVE := 8;    --number of inputs
5          N: POSITIVE := 4);   --size of each input
6      PORT (
7          x: IN BIT_VECTOR (M*N-1 DOWNT0 0);
8          sel: IN NATURAL RANGE 0 TO M-1;
9          y: OUT BIT_VECTOR(N-1 DOWNT0 0));
10  END ENTITY;
11  -----
12  ARCHITECTURE arch2 OF generic_mux IS
13  BEGIN
14      gen: FOR i IN N-1 DOWNT0 0 GENERATE
15          y(i) <= x(N*sel+i);
16      END GENERATE gen;
17  END ARCHITECTURE;
18  -----

```

Exercise 6.1: Latch and flip-flop

a) See figure below.

 


b) VHDL code and simulation:

```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY example IS
6      PORT (
7          d, clk: IN STD_LOGIC;
8          q1, q2: OUT STD_LOGIC);
9  END ENTITY;
10 -----
11 ARCHITECTURE example OF example IS
12 BEGIN
13     PROCESS(clk, d)
14     BEGIN
15         ---Latch:-----
16         IF clk='1' THEN
17             q1 <= d;
18         END IF;
19         ---Flip-flop:----
20         IF clk'EVENT AND clk='1' THEN --or IF rising_edge(clk) THEN
21             q2 <= d;
22         END IF;
23     END PROCESS;
24 END ARCHITECTURE;
25 -----

```


Simulation results:

 

Exercise 6.4: Generic registered multiplexer

Just add a register (N flip-flops) to the output of the mux designed in exercise 5.20 (recall that now a process is needed).

Exercise 6.8: Signal generator

 

Two additional waveforms (a, b) were included in the figure. Note that there is a big difference between generating a, b versus x, y , because each signal in the former pair changes its state always at the same clock edge, so its resolution is one clock period, while in the latter pair each signal can change at both clock transitions, so with a resolution equal to one-half of a clock period (which is the maximum resolution in digital systems). In the code below, first a and b are generated, then

trivial logic gates are employed to obtain x and y . Note that this implementation is free from glitches because only two signals enter the gates, and such signals can never change at the same time (they operate at different clock edges).

```

1  -----
2  ENTITY signal_generator IS
3      PORT (
4          clk: IN BIT;
5          x, y: OUT BIT);
6  END ENTITY;
7  -----
8  ARCHITECTURE arch OF signal_generator IS
9  BEGIN
10     PROCESS(clk)
11         VARIABLE a, b: BIT;
12     BEGIN
13         IF clk'EVENT AND clk='1' THEN --or IF rising_edge(clk) THEN
14             a := NOT a;
15         ELSIF clk'EVENT AND clk='0' THEN --or ELSIF falling_edge(clk) THEN
16             b := NOT a;
17         END IF;
18         x <= a AND b;
19         y <= a NOR b;
20     END PROCESS;
21 END ARCHITECTURE;
22 -----

```

Exercise 6.9: Switch debouncer

```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY debouncer IS
6      GENERIC(
7          fclk: NATURAL := 50;          --clock freq in MHz
8          twindow: NATURAL := 10);    --time window in ms
9      PORT (
10         sw: IN STD_LOGIC;
11         clk: IN STD_LOGIC;
12         deb_sw: BUFFER STD_LOGIC);
13 END ENTITY;
14 -----
15 ARCHITECTURE digital_debouncer OF debouncer IS
16     CONSTANT max: NATURAL := 1000 * fclk * twindow;
17 BEGIN
18     PROCESS (clk)
19         VARIABLE count: NATURAL RANGE 0 TO max;
20     BEGIN
21         IF (clk'EVENT AND clk='1') THEN --or IF rising_edge(clk) THEN
22             IF (deb_sw /= sw) THEN
23                 count := count + 1;
24                 IF (count=max) THEN
25                     deb_sw <= sw;
26                     count := 0;
27                 END IF;
28             ELSE
29                 count := 0;
30             END IF;
31         END IF;
32     END PROCESS;
33 END ARCHITECTURE;
34 -----

```

Exercise 6.12: Programmable signal generator

(Note: See a continuation for this design in exercise 6.13.)

a) The dividers must be even if we want to operate in only one (say, rising) clock edge (if the clock's duty cycle is unknown that is the only option).

$50\text{MHz}/10\text{kHz} = 5000$ (error = 0 Hz)

50MHz/9kHz = 5555.55 (use 5556 → 50M/5556 = 8999.28, so error = -0.72 Hz)
 50MHz/8kHz = 6250 (error = 0 Hz)
 50MHz/7kHz = 7142.86 (use 7142 → 50M/7142 = 7000.84, so error = 0.84 Hz)
 50MHz/6kHz = 8333.33 (use 8334 → 50M/8334 = 5999.52, so error = -0.48 Hz)
 50MHz/5kHz = 10000 (error = 0 Hz)
 50MHz/4kHz = 12500 (error = 0 Hz)
 50MHz/3kHz = 16666.66 (use 16666 → 50M/16666 = 3000.12, so error = 0.12 Hz)
 50MHz/2kHz = 25000 (error = 0 Hz)
 50MHz/1kHz = 50000 (error = 0 Hz)


b) VHDL code:

Note the use of “>=” rather than “=” in the “count>=divider/2” test. This is needed for the counter to immediately shift to the new mode in case the counter already is above “count=divider/2” when the test is done (otherwise, we would need to wait until the counter reached its full scale, after which it would automatically restart from zero).

```

1  -----
2  ENTITY sig_generator IS
3      GENERIC (
4          fclk: POSITIVE := 50_000_000);
5      PORT (
6          clk, freq: IN BIT;
7          sig_out: BUFFER BIT);
8  END ENTITY;
9  -----
10 ARCHITECTURE sig_generator OF sig_generator IS
11     TYPE ROM IS ARRAY (0 TO 3) OF POSITIVE RANGE 1 TO 8;
12     CONSTANT coefficients: ROM := (8, 6, 4, 2);
13     SIGNAL divider: POSITIVE RANGE 1 TO 8;
14 BEGIN
15     PROCESS (freq)
16         VARIABLE i: NATURAL RANGE 0 TO 4;
17     BEGIN
18         IF (freq'EVENT AND freq='1') THEN --or IF rising_edge(freq) THEN
19             i := i + 1;
20             IF (i=4) THEN
21                 i := 0;
22             END IF;
23             divider <= coefficients(i);
24         END PROCESS;
25     -----
26     PROCESS (clk)
27         VARIABLE count: NATURAL RANGE 0 TO 4;
28     BEGIN
29         IF (clk'EVENT AND clk='1') THEN --or IF rising_edge(clk) THEN
30             count := count + 1;
31             IF (count>=divider/2) THEN --It is ">="
32                 count := 0;
33                 sig_out <= NOT sig_out;
34             END IF;
35         END IF;
36     END PROCESS;
37 END ARCHITECTURE;
38 -----
39 -----
  
```


c) Simulation results:

 

Exercise 6.13: Programmable Signal Generator with Frequency Meter

- a) See circuits and code in section 22.5 of [Pedroni 2008]. Adopt the implementation in Fig. 22.9(a).
- b) Put the code of part (a) above together with the code of exercise 6.12 to attain the complete system. Another option (not discussed yet) is to use the COMPONENT construct (described in chapter 8), in which case the main code can be constructed with just two lines (two component instantiations).
- c) This implementation in the FPGA board is a very interesting and stimulating design demonstration.

Exercise 7.3: Latches and flip-flops

 

Code 1: This is a D-type latch with asynchronous reset (figure (a) above). Note that, contrary to flip-flop implementations, *d* needs to be in the sensitivity list because the circuit is transparent during a whole semi-period of the clock, not just during the clock transition. (Even though the compiler might understand from the context that a latch is wanted even if *d* is not in the sensitivity list, that is not a good practice.)

Code 2: Now we have a D-type flip-flop instead of a D-type latch (note the 'EVENT attribute). Because reset is only activated when a (positive) clock edge occurs, it is *synchronous*; since in our context an asynchronous reset is an actual reset, while a synchronous reset is indeed a *clear* signal, the proper circuit is that of figure (b).

Code 3: This is an example of bad design. In principle, it seems that a latch with clear is wanted, like that in figure (c). However, because only *clk* is in the sensitivity list, the process will only be run when *clk* changes, which emulates the behavior of a flip-flop. In summary, the flip-flop of figure (b) might be inferred.

Exercise 7.4: Combinational versus sequential circuits #1

- a) It is combinational because the output depends solely on the current input.
- b) According to Rule 6 in figure 7.1, registers are inferred when a value is assigned to a signal at the transition of another signal (normally using the 'EVENT attribute; or, equivalently, the *rising_edge* or *falling_edge* function), which does not happen in this code.
- c) Same as (a) above.
- d) Same as (b) above.

Exercise 7.7: Registered circuits

- a) Code analysis:


Code 1 is a 8x1 multiplexer (8 inputs, 1 bit each), implemented by line 14, followed by a one-bit register. Hence only one DFF is needed. The compiled circuit is shown in figure (a) below.

Code 2 is the opposite, that is, it contains a register (8 bits, so 8 DFFs are needed, inferred by lines 14-16) followed by an 8x1 mux (line 17). The compiled circuit is in figure (b).

Code 3 is similar to code 1. The only difference is that no internal signal was used to implement the multiplexer (it was implemented directly in line 14). Hence the circuit is that of figure (a), with one DFF.

- b) Compilation: The inferred circuits are in the figure below.

c) Codes 1 and 3 implement the same circuit. The hardwares inferred from these two codes are equal, so from the implementation point-of-view there are no differences between them. However, code 3 is more compact, while code 1 makes it clearer that a mux followed by a register is the wanted circuit.

 

Exercise 7.9: Frequency divider with VARIABLE

a) Number of flip-flops:

An M -state counter (from 0 to $M-1$, for example) can be used to solve this problem, so the number of DFFs is $\lceil \log_2 M \rceil$ for the counter, plus one to store clk_out . For example, for $M=4$ or $M=5$, 3 or 4 DFFs are needed, respectively.


b) VHDL code (see simulation results in the figure that follows):

```

1  -----
2  ENTITY clock_divider IS
3      GENERIC (
4          M: NATURAL := 5;
5      PORT (
6          clk_in: IN BIT;
7          clk_out: OUT BIT);
8  END ENTITY;
9  -----
10 ARCHITECTURE circuit OF clock_divider IS
11 BEGIN
12     PROCESS (clk_in)
13         VARIABLE counter: NATURAL RANGE 0 TO M;
14     BEGIN
15         IF clk_in'EVENT AND clk_in='1' THEN --or IF rising_edge(clk_in) THEN
16             counter := counter + 1;
17             IF counter=M/2 THEN
18                 clk_out <= '1';
19             ELSIF counter=M THEN
20                 clk_out <= '0';
21                 counter := 0;
22             END IF;
23         END IF;
24     END PROCESS;
25 END ARCHITECTURE;
26 -----


```

Simulation results for $M=5$:

 

c) Because a DFF is used to store clk_out (so this signal comes directly from a flip-flop), it is automatically free from glitches.

 Exercise 8.6: Synchronous counter with COMPONENT



a) The standard cell is illustrated on the left-hand side of the figure above. A corresponding VHDL code follows, using *method 1*.

```

1  ----The component:-----
2  ENTITY counter_cell IS
3      PORT (
4          clk, a, b: IN BIT;
5          c, q: BUFFER BIT);
6  END ENTITY;
7  -----
8  ARCHITECTURE counter_cell OF counter_cell IS
9      SIGNAL d: BIT;
10 BEGIN
11     PROCESS (clk, a, b)
12     BEGIN
13         c <= a AND b;
14         d <= c XOR q;
15         IF clk'EVENT AND clk='1' THEN
16             q <= d;
17         END IF;
18     END PROCESS;
19 END ARCHITECTURE;
20 -----


1  ----Main code:-----
2  ENTITY N_bit_counter IS
3      GENERIC (
4          N: NATURAL := 4); --number of bits
5      PORT (
6          clk: IN BIT;
7          q: OUT BIT_VECTOR(0 TO N-1));
8  END ENTITY;
9  -----
10 ARCHITECTURE structural OF N_bit_counter IS
11     SIGNAL a, b: BIT_VECTOR(0 TO N);
12     --component declaration:--
13     COMPONENT counter_cell IS
14         PORT (
15             clk, a, b: IN BIT;
16             c, q: BUFFER BIT);
17     END COMPONENT;
18 BEGIN
19     a(0) <= '1';
20     b(0) <= '1';
21     gen: FOR i IN 0 TO N-1 GENERATE
22         counter: counter_cell PORT MAP (clk, a(i), b(i), a(i+1), b(i+1));
23     END GENERATE;
24     q <= b(1 TO N);
25 END ARCHITECTURE;
26 -----

```

b) Having seen the code for *method 1*, doing it for *method 3* is straightforward (see example 8.4).

 Exercise 8.8: Tapped delay line with COMPONENT and GENERIC MAP

The “standard” cells can be seen in the figure below. Each cell contains an M -stage (so the cell is not truly standard) shift register followed by a multiplexer. The latter selects either the cell input (if $sel \neq '0'$), hence without delay, or the cell output (when $sel = '1'$), hence with a delay of M clock cycles. The figure also shows the signal names, as used in the VHDL code that follows (int =interface, sel =select, etc.). The circuit produced by the compiler is depicted in the figure after the code.



```

1  ----The component:-----
2  ENTITY delay_cell IS

```


```

3     GENERIC (
4         M: NATURAL);
5     PORT (
6         d, clk, rst, sel: IN BIT;
7         q: OUT BIT);
8 END ENTITY;
9 -----
10 ARCHITECTURE delay_cell OF delay_cell IS
11     SIGNAL internal: BIT_VECTOR(0 TO M-1);
12 BEGIN
13     PROCESS (clk, rst)
14     BEGIN
15         IF (rst='1') THEN
16             internal <= (OTHERS => '0');
17         ELSIF (clk'EVENT AND clk='1') THEN
18             IF (M=1) THEN
19                 internal(0) <= d;
20             ELSE
21                 internal <= d & internal(0 TO M-2);
22             END IF;
23         END IF;
24     END PROCESS;
25     q <= d WHEN sel='0' ELSE internal(M-1);
26 END ARCHITECTURE;
27 -----

1  ---Main code:-----
2 ENTITY tapped_delay_line IS
3     GENERIC (
4         M: NATURAL := 4);
5     PORT (
6         d, clk, rst: IN BIT;
7         sel: IN BIT_VECTOR(2 DOWNTO 0);
8         q: OUT BIT);
9 END ENTITY;
10 -----
11 ARCHITECTURE structural OF tapped_delay_line IS
12     SIGNAL int: BIT_VECTOR(2 DOWNTO 0);
13     --component declaration:
14     COMPONENT delay_cell IS
15         GENERIC (
16             M: NATURAL);
17         PORT (
18             d, clk, rst, sel: IN BIT;
19             q: OUT BIT);
20     END COMPONENT;
21 BEGIN
22     cell2: delay_cell GENERIC MAP (M=>4) PORT MAP (d, clk, rst, sel(2), int(2));
23     cell1: delay_cell GENERIC MAP (M=>2) PORT MAP (int(2), clk, rst, sel(1), int(1));
24     cell0: delay_cell GENERIC MAP (M=>1) PORT MAP (int(1), clk, rst, sel(0), int(0));
25     q <= int(0);
26 END ARCHITECTURE;
27 -----

```

Result shown by the RTL Viewer:

 

Exercise 9.1: ASSERT statement #1

Just include the code below between lines 15-16 of the package.

```

ASSERT (a'LENGTH=b'LENGTH)
REPORT "Signals a and b do not have the same length!"
SEVERITY FAILURE;

```

Note: There is a typo in example 9.5; remove the semi-colon at the end of line 18.

Exercise 9.5: Function *my_not*

A code for this problem is shown below (note that it is similar to that in example 9.6). The function *my_not* was created in a package, then used in the main code to invert a vector *x*, passing the result to *y*. An alias was employed for *a* in order to make the code independent from the range indexes employed to specify the function input. For instance, note the unusual ranges used for *x* and *y* in the main code, with only are fine because the alias *aa* was adopted.

```

1  ----Package:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  PACKAGE my_package IS
6      FUNCTION my_not (a: STD_LOGIC_VECTOR) RETURN STD_LOGIC_VECTOR;
7  END PACKAGE;
8  -----
9  PACKAGE BODY my_package IS
10     TYPE stdlogic_1d IS ARRAY (STD_ULOGIC) OF STD_ULOGIC;
11     CONSTANT not_table: stdlogic_1d :=
12         -----
13         -- U    X    0    1    Z    W    L    H    -
14         -----
15         ( 'U', 'X', '1', '0', 'X', 'X', '1', '0', 'X');
16         -----
17     FUNCTION my_not (a: STD_LOGIC_VECTOR) RETURN STD_LOGIC_VECTOR IS
18         ALIAS aa: STD_LOGIC_VECTOR(1 TO a'LENGTH) IS a;
19         VARIABLE result: STD_LOGIC_VECTOR(1 TO a'LENGTH);
20     BEGIN
21         FOR i IN result'RANGE LOOP
22             result(i) := not_table (aa(i));
23         END LOOP;
24         RETURN result;
25     END FUNCTION;
26 END PACKAGE BODY;
27 -----

1  ----Main code:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE work.my_package.all;
5  -----
6  ENTITY test IS
7      PORT (
8          x: IN STD_LOGIC_VECTOR(8 DOWNTO 1);
9          y: OUT STD_LOGIC_VECTOR(2 TO 9));
10 END ENTITY;
11 -----
12 ARCHITECTURE example OF test IS
13 BEGIN
14     y <= my_not(x);
15 END ARCHITECTURE;
16 -----

```


Exercise 9.6: Function *bcd_to_ssd*

See the function *integer_to_ssd* in section 2.5. The ASSERT statement can be based on the solution for exercise 9.1.

 Exercise 10.1: Generation of periodic stimuli

All three signals are depicted in the figure below, followed by a VHDL code that produces all three.

Note that the WAIT FOR statement was used in this solution. The reader is invited to redo it using AFTER. Which is simpler in this case?




```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY stimuli_generator IS
6  END ENTITY;
7  -----
8  ARCHITECTURE testbench OF stimuli_generator IS
9      SIGNAL sig1, sig2, y: STD_LOGIC;
10 BEGIN
11     PROCESS
12     BEGIN
13         --signal sig1:--
14         sig1 <= '1';
15         WAIT FOR 25ns;
16         sig1 <= '0';
17         WAIT FOR 50ns;
18         --signal sig2:--
19         sig2 <= '1';
20         WAIT FOR 25ns;
21         sig2 <= '0';
22         WAIT FOR 50ns;
23         sig2 <= '1';
24         WAIT FOR 25ns;
25         sig2 <= '0';
26         WAIT FOR 25ns;
27         sig2 <= '1';
28         WAIT FOR 50ns;
29         sig2 <= '0';
30         WAIT FOR 25ns;
31         --signal y:--
32         y <= '1';
33         WAIT FOR 20ns;
34         y <= '0';
35         WAIT FOR 10ns;
36         y <= '1';
37         WAIT FOR 10ns;
38         y <= '0';
39         WAIT FOR 40ns;
40     END PROCESS;
41 END ARCHITECTURE;
42 -----

```

 Exercise 10.11: Type I testbench for an address decoder

The simulation stimuli (*ena* and *address*) to be used in this exercise are those of example 2.4 (figure 2.7), repeated in the figure below. The expected *functional* response (*wordline*) derived from them is also included in the figure.



A corresponding design file (*address_decoder.vhd*) is presented next. Notice that only STD_LOGIC data (lines 8-10) was employed, which is the industry standard. Observe also that this code is totally generic; to implement an address decoder of any size, the only change needed is in line 7.

The circuit can be designed in several ways. Here, concurrent code (with GENERATE and WHEN) was employed. Another option can be seen in the solutions for the 1st edition of the book.

```

1  -----Design file (address_decoder.vhd):-----

```

```

2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE ieee.std_logic_unsigned.all;
5  -----
6  ENTITY address_decoder IS
7      GENERIC (
8          N: NATURAL := 3); --number of input bits
9      PORT (
10         ena: STD_LOGIC;
11         address: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
12         wordline: OUT STD_LOGIC_VECTOR(2*N-1 DOWNT0 0));
13 END ENTITY;
14 -----
15 ARCHITECTURE decoder OF address_decoder IS
16     SIGNAL addr: NATURAL RANGE 0 TO 2*N-1;
17 BEGIN
18     addr <= CONV_INTEGER(address);
19     gen: FOR i IN 0 TO 2*N-1 GENERATE
20         wordline(i) <= '1' WHEN ena='0' ELSE
21                     '0' WHEN i=addr ELSE
22                     '1';
23     END GENERATE;
24 END ARCHITECTURE;
25 -----

```


VHDL code for a type I testbench (file *address_decoder_tb.vhd*) is shown next. The input waveforms are those in the previous figure, with $T = 80$ ns (line 9). The code construction is similar to that seen in section 10.8 (example 10.4). The statement in line 34 guarantees that after a certain time (800 ns in this example – see line 10) the simulation will end.

```

1  -----Testbench file (address_decoder_tb.vhd):-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE ieee.std_logic_unsigned.all;
5  -----
6  ENTITY address_decoder_tb IS
7      GENERIC (
8          N: NATURAL := 3;          --# of bits at input
9          T: TIME := 80 ns;        --stimulus period
10         Tfinal: TIME := 800 ns); --end of simulation time
11 END ENTITY;
12 -----
13 ARCHITECTURE testbench OF address_decoder_tb IS
14     --Signal declarations:----
15     SIGNAL ena_tb: STD_LOGIC := '0';
16     SIGNAL address_tb: STD_LOGIC_VECTOR(N-1 DOWNT0 0) := (OTHERS => '0');
17     SIGNAL wordline_tb: STD_LOGIC_VECTOR(2*N-1 DOWNT0 0); --from circuit
18     --DUT declaration:-----
19     COMPONENT address_decoder IS
20         PORT (
21             ena: STD_LOGIC;
22             address: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
23             wordline: OUT STD_LOGIC_VECTOR(2*N-1 DOWNT0 0));
24     END COMPONENT;
25 BEGIN
26     --DUT instantiation:-----
27     dut: address_decoder PORT MAP (ena_tb, address_tb, wordline_tb);
28     --Generate enable:
29     ena_tb <= '1' AFTER T;
30     --Generate address:-----
31     PROCESS
32     BEGIN
33         WAIT FOR T;
34         WHILE NOW<Tfinal LOOP --this loop could be unconditional
35             WAIT FOR T;
36             IF (address_tb < 2*N-1) THEN
37                 address_tb <= address_tb + 1;
38             ELSE
39                 address_tb <= (OTHERS => '0');
40             END IF;
41         END LOOP;
42     END PROCESS;
43 END ARCHITECTURE;
44 -----

```



Simulation results (from ModelSim) are shown in the next figure. Note that, being it a type I (therefore functional) simulation, there are no propagation delays between the transitions of *address_tb* and *wordline_tb*. Observe also that the result produced by the circuit (*wordline_tb*) does match the expected result (*wordline*) shown in the previous figure.

 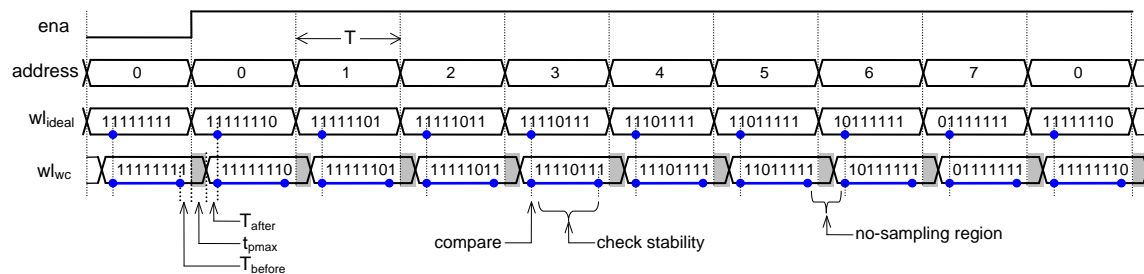

Exercise 10.12: Type IV testbench for an address decoder

Note: Before examining this solution, please read the item “Additional Details on Type IV Simulation” in the “Extra Material” link of the book website.

The simulation stimuli (*ena* and *address*) to be used in this exercise are those of example 2.4 (figure 2.7), repeated in the figure below. From them, the expected *functional* response (ideal wordline, wl_{ideal}) is that also included in the figure, already seen in the solution to exercise 10.11. The last waveform (worst-case wordline, wl_{wc}) is the signal expected to be produced by the circuit, which will be used as a reference to define the comparison points and stability test intervals.



The design file (*address_decoder.vhd*) is the same seen in the previous exercise. A corresponding testbench file (*address_decoder_tb.vhd*) for type IV simulation is presented below. The maximum propagation delay for the device used in this project (a Cyclone II FPGA, from Altera, synthesized with Quartus II; for Xilinx devices, ISE would be the natural choice) was approximately 13 ns, so $t_{pmax}=15$ ns was adopted (line 10). The stimulus (*address*) period is 80 ns (line 9), and both time margins are 1 ns (lines 11-12). The total simulation time is 800 ns (line 13).

The simulation procedure is that described in chapter 10 and appendix D (must include the SDF and delay-annotated files). See section 10.11 and example 10.6 for additional details.

```

1  --Testbench file (address_decoder_tb.vhd)-----
2  --Note 1: Because GENERIC parameters cannot be passed to the .vho file, if the value of
3  --N below must be changed, then the design must be resynthesized to get a new .vho file.
4  LIBRARY ieee;
5  USE ieee.std_logic_1164.all;
6  USE ieee.std_logic_arith.all;
7  -----
8  ENTITY address_decoder_tb IS
9      GENERIC (
10         N: NATURAL := 3;           --# of bits at input (see Note 1 above)
11         T: TIME := 80 ns;         --stimulus period
12         tpmax: TIME := 15 ns;      --maximum propagation delay
13         Tbefore: TIME := 1 ns;     --time margin before transition
14         Tafter: TIME := 1 ns;      --time margin after transition
15         Tfinal: TIME := 800 ns);  --end of simulation
16  END ENTITY;
17  -----
18  ARCHITECTURE testbench OF address_decoder_tb IS
19      --Constant and signal declarations:-----
20      CONSTANT T1: TIME := Tpmax + Tafter;  --16ns
21      CONSTANT T2: TIME := T - T1 - Tbefore; --63ns
22      SIGNAL ena_tb: STD_LOGIC := '0';
23      SIGNAL address_tb: STD_LOGIC_VECTOR(N-1 DOWNT0 0) := (OTHERS => '0');
24      SIGNAL wordline_ideal: STD_LOGIC_VECTOR(2*N-1 DOWNT0 0) := (OTHERS => '1'); --ideal
25      SIGNAL wordline_tb: STD_LOGIC_VECTOR(2*N-1 DOWNT0 0); --actual circuit output


```

```

26  --DUT declaration:-----
27  COMPONENT address_decoder IS  --see Note 1 above
28      PORT (
29          ena: STD_LOGIC;
30          address: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0);
31          wordline: OUT STD_LOGIC_VECTOR(2**N-1 DOWNT0 0));
32  END COMPONENT;
33  BEGIN
34      --DUT instantiation (see Note 1 above):-----
35      dut: address_decoder PORT MAP (ena_tb, address_tb, wordline_tb);
36      --Generate enable:-----
37      ena_tb <= '1' AFTER T;
38      --Generate address + expected ideal output:--
39      PROCESS
40          VARIABLE count: NATURAL RANGE 0 TO 2**N-1 := 0;
41      BEGIN
42          WAIT FOR T;
43          WHILE NOW<Tfinal LOOP --this loop could be unconditional
44              address_tb <= conv_std_logic_vector(count, N);
45              wordline_ideal <= (count=>'0', OTHERS=>'1');
46              WAIT FOR T;
47              IF (count < 2**N-1) THEN
48                  count := count + 1;
49              ELSE
50                  count := 0;
51              END IF;
52          END LOOP;
53      END PROCESS;
54      --Comparison + stability test:-----
55      PROCESS
56      BEGIN
57          IF (NOW<Tfinal) THEN
58              WAIT FOR T1;
59              ASSERT (wordline_tb=wordline_ideal)
60                  REPORT "Error: Signal values are not equal!"
61                  SEVERITY FAILURE;
62              WAIT FOR T2;
63              ASSERT wordline_tb'STABLE(T2)
64                  REPORT "Error: Signal is unstable!"
65                  SEVERITY FAILURE;
66              WAIT FOR Tbefore;
67          ELSE
68              ASSERT FALSE
69                  REPORT "END OF SIMULATION: No error found!"
70                  SEVERITY FAILURE;
71          END IF;
72      END PROCESS;
73  END ARCHITECTURE;
74  -----

```

 
Simulation results are depicted in the figure below. Observe that the actual output (*wordline_tb*) does exhibit propagation delays (of the order of 13 ns for the chosen device) after corresponding address (*address_tb*) transitions.



The following (very important) challenges are left to the reader:

- 1) To play with the testbench file. For example, what happens if the value of t_{pmax} is reduced to a value below the actual propagation delay (say, 8 ns)? And what happens if line 60 is changed to "ASSERT wordline_tb'STABLE(T2 + 5 ns) . . ."?
- 2) To include in the ASSERT statements the code needed for the simulator to display the time value and the signal values in case an error is found (as in example 10.6).

Exercise 11.4: Zero-to-nine counter

 

The adjusted state transition diagram is shown above. The only difference is that $T (=1s)$ is now a condition for the system to progress from one state to another (see *timed machines* in section 11.6). A corresponding VHDL code is shown below. T was set to 50M, which was assumed to be the clock frequency, so the system changes its state after every second. The SSD was considered to be a common-anode display (so a '0' lights a segment, while a '1' turns it off). See additional comments after the code.

```

1  -----
2  ENTITY slow_counter IS
3      GENERIC (
4          T: NATURAL := 50_000_000); --T=fclk -> 1s
5      PORT (
6          clk, rst: IN BIT;
7          output: OUT BIT_VECTOR(6 DOWNTO 0));
8  END ENTITY;
9  -----
10 ARCHITECTURE fsm OF slow_counter IS
11     TYPE state IS (zero, one, two, three, four, five,
12                   six, seven, eight, nine);
13     SIGNAL pr_state, nx_state: state;
14     SIGNAL counter_output: NATURAL RANGE 0 TO 9;
15 BEGIN
16     ----Lower section of FSM:-----
17     PROCESS (rst, clk)
18         VARIABLE count: NATURAL RANGE 0 TO T;
19     BEGIN
20         IF (rst='1') THEN
21             pr_state <= zero;
22         ELSIF (clk'EVENT AND clk='1') THEN
23             count := count + 1;
24             IF (count=T) THEN
25                 count := 0;
26                 pr_state <= nx_state;
27             END IF;
28         END IF;
29     END PROCESS;
30     ----Upper section of FSM:-----
31     PROCESS (pr_state)
32     BEGIN
33         CASE pr_state IS
34             WHEN zero =>
35                 counter_output <= 0;
36                 nx_state <= one;
37             WHEN one =>
38                 counter_output <= 1;
39                 nx_state <= two;
40             WHEN two =>
41                 counter_output <= 2;
42                 nx_state <= three;
43             WHEN three =>
44                 counter_output <= 3;
45                 nx_state <= four;
46             WHEN four =>
47                 counter_output <= 4;
48                 nx_state <= five;
49             WHEN five =>
50                 counter_output <= 5;
51                 nx_state <= six;
52             WHEN six =>
53                 counter_output <= 6;
54                 nx_state <= seven;
55             WHEN seven =>
56                 counter_output <= 7;
57                 nx_state <= eight;
58             WHEN eight =>
59                 counter_output <= 8;
60                 nx_state <= nine;

```

```

61         WHEN nine =>
62             counter_output <= 9;
63             nx_state <= zero;
64         END CASE;
65     END PROCESS;
66     ----BCD-to-SSD converter:-----
67     PROCESS (counter_output)
68     BEGIN
69         CASE counter_output IS
70             WHEN 0 => output<="0000001"; --"0" on SSD
71             WHEN 1 => output<="1001111"; --"1" on SSD
72             WHEN 2 => output<="0010010"; --"2" on SSD
73             WHEN 3 => output<="0000110"; --"3" on SSD
74             WHEN 4 => output<="1001100"; --"4" on SSD
75             WHEN 5 => output<="0100100"; --"5" on SSD
76             WHEN 6 => output<="0100000"; --"6" on SSD
77             WHEN 7 => output<="0001111"; --"7" on SSD
78             WHEN 8 => output<="0000000"; --"8" on SSD
79             WHEN 9 => output<="0000100"; --"9" on SSD
80             WHEN OTHERS => output<="0110000"; --"E"rror
81         END CASE;
82     END PROCESS;
83 END ARCHITECTURE;
84 -----

```


To make the implementation clearer, the BCD-to-SSD converter (SSD driver) was implemented in a separate process, but it could be nested inside the code for the upper section of the FSM, as shown below:

```

-----
CASE pr_state IS
  WHEN zero =>
    output <= "0000001";
    nx_state <= one;
  WHEN one =>
    output <= "1001111";
    nx_state <= two;
  ...
-----

```

Exercise 11.6: Signal generator #2

 

a) The state transition diagram is included in the figure above. A 0-to-39 counter was chosen to control the state transitions (it counts from 0-to-19 in one state, hence 20 clock periods, then 0-to-39 in the other state, thus 40 clock cycles), but recall that any counter with 40 states would do [Pedroni 2008]. Another option would be to use a 60-state counter, which would only be reset after reaching 59. A VHDL code for the state machine shown in the figure is presented below. Because the output coincides with the state representation (that is, $output=pr_state$), the output comes directly from a flip-flop, so the circuit is automatically glitch-free. (Suggestion: to ease the inspection of the simulation results use 2 and 4 instead of 20 and 40 for the generic parameters *PulsesLow* and *PulsesHigh*, respectively.)

```

1  -----
2  ENTITY signal_generator IS
3      GENERIC (
4          PulsesLow: NATURAL := 20;    --time in state OutputLow
5          PulsesHigh: NATURAL := 40);  --time in state OutputHigh
6      PORT (
7          clk, rst: IN BIT;
8          output: OUT BIT);
9  END ENTITY;
10 -----
11 ARCHITECTURE fsm OF signal_generator IS
12     TYPE state IS (OutputLow, OutputHigh);
13     SIGNAL pr_state, nx_state: state;
14     SIGNAL number_of_pulses: NATURAL RANGE 0 TO PulsesHigh;
15 BEGIN
16     ----Lower section of FSM:-----


```

```

17  PROCESS (rst, clk)
18      VARIABLE count: NATURAL RANGE 0 TO PulsesHigh;
19  BEGIN
20      IF (rst='1') THEN
21          pr_state <= OutputLow;
22      ELSIF (clk'EVENT AND clk='1') THEN
23          count := count + 1;
24          IF (count=number_of_pulses) THEN
25              count := 0;
26              pr_state <= nx_state;
27          END IF;
28      END IF;
29  END PROCESS;
30  ----Upper section of FSM:-----
31  PROCESS (pr_state)
32  BEGIN
33      CASE pr_state IS
34          WHEN OutputLow =>
35              output <= '0';
36              number_of_pulses <= PulsesLow;
37              nx_state <= OutputHigh;
38          WHEN OutputHigh =>
39              output <= '1';
40              number_of_pulses <= PulsesHigh;
41              nx_state <= OutputLow;
42      END CASE;
43  END PROCESS;
44  END ARCHITECTURE;
45  -----

```

 Exercise 11.11: Preventing state-bypass with a flag #2



This exercise deals with a crucial aspect of state machines: *state bypass*. This problem arises when we want the machine to stay in a certain state until a predefined condition “re-occurs”.

In figure (a) above, if the machine is in state A and a long $x=1$ occurs, it goes to B, then moves immediately to C at the next clock edge (that is, it stays in B during only one clock period). Sometimes this is exactly what we want, so there is no actual state bypass. However, in many cases (like the car alarm seen in section 11.5), we want the machine to proceed to the next state only if a certain condition happens *anew*. For example, in figure (b), the machine moves from A to B if $x=1$; after arriving in B, only if a *new* $x=1$ occurs it should move to C, thus requiring x to return to ‘0’ before a state transition is again considered. A VHDL code for that FSM (with a flag) is presented below. Simulation results are shown subsequently.

Note: In some applications the machine is only required to stay in certain (or all) states for a certain amount of time (that is, a certain number of clock cycles) before the input conditions are again evaluated. This must not be confused with the state-bypass problem, because this is simply a *timed* machine (described in section 11.6).

```

1  -----
2  ENTITY fsm_without_bypass IS
3      PORT (
4          clk, rst, x: IN BIT;
5          y: OUT BIT);
6  END ENTITY;
7  -----
8  ARCHITECTURE fsm OF fsm_without_bypass IS
9      TYPE state IS (A, B, C);
10     SIGNAL pr_state, nx_state: state;
11     ATTRIBUTE enum_encoding: STRING;
12     ATTRIBUTE enum_encoding OF state: TYPE IS "sequential";
13     SIGNAL flag: BIT;
14  BEGIN
15     ----Flag generator:-----


```

```


16  PROCESS (clk, rst)
17  BEGIN
18      IF (rst='1') THEN
19          flag <= '0';
20      ELSIF (clk'EVENT AND clk='1') THEN
21          IF (x='0') THEN
22              flag <= '1';
23          ELSE
24              flag <= '0';
25          END IF;
26      END IF;
27  END PROCESS;
28  ----Lower section of FSM:-----
29  PROCESS (rst, clk)
30  BEGIN
31      IF (rst='1') THEN
32          pr_state <= A;
33      ELSIF (clk'EVENT AND clk='1') THEN
34          pr_state <= nx_state;
35      END IF;
36  END PROCESS;
37  ----Upper section of FSM:-----
38  PROCESS (pr_state, x, flag)
39  BEGIN
40      CASE pr_state IS
41          WHEN A =>
42              y <= '0';
43              IF (x='1' AND flag='1') THEN nx_state <= B;
44              ELSE nx_state <= A;
45              END IF;
46          WHEN B =>
47              y <= '0';
48              IF (x='1' AND flag='1') THEN nx_state <= C;
49              ELSE nx_state <= B;
50              END IF;
51          WHEN C =>
52              y <= '1';
53              IF (x='0') THEN nx_state <= A;
54              ELSE nx_state <= C;
55              END IF;
56      END CASE;
57  END PROCESS;
58  END ARCHITECTURE;
59  -----

```

 The view produced by the state machine viewer (with the *enum_encoding* attribute commented out) is shown below.



Simulation results:

 

Exercise 11.15: FSM with embedded timer #2

First we need to clarify the diagram above. There are two options for the timed transitions (B-C and C-A). Taking the B-C transition, for example, the specifications can be the as follows.

- i) The machine must stay *time1* seconds in B and then evaluate x; if x=2 after that time interval, then the machine must proceed to state C.
- ii) The value of x must be x=2 for at least *time1* seconds; therefore, if x changes its value before *time1* has been completed, the time counting must restart.


Both options can occur, depending on the application. In the present solution, we will consider that case (ii) is wanted. A corresponding VHDL code follows. Note that because the "pr_state <= nx_state;" assignment only occurs when all conditions are met, there is no need for specifying other next states besides the actual next state in each state specifications (that is, in state A, the only possible next state is B; in B, it is C; and in C, it is A).

```

1  -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY fsm IS
6      GENERIC (
7          time1: NATURAL := 3; -- # of clock periods in B
8          time2: NATURAL := 4); -- # of clock periods in C
9      PORT (
10         clk, rst: IN STD_LOGIC;
11         x: IN NATURAL RANGE 0 TO 3;
12         y: OUT STD_LOGIC);
13  END ENTITY;
14  -----
15  ARCHITECTURE fsm OF fsm IS
16      TYPE state IS (A, B, C);
17      SIGNAL pr_state, nx_state: state;
18      ATTRIBUTE enum_encoding: STRING;
19      ATTRIBUTE enum_encoding OF state: TYPE IS "sequential";
20      SIGNAL T: NATURAL RANGE 0 TO time2;
21      SIGNAL input1, input2: NATURAL RANGE x'RANGE;
22  BEGIN
23      ----Lower section of FSM:-----
24      PROCESS (rst, clk)
25          VARIABLE count: NATURAL RANGE 0 TO time2;
26      BEGIN
27          IF (rst='1') THEN
28              pr_state <= A;
29          ELSIF (clk'EVENT AND clk='1') THEN
30              IF (x=input1 OR x=input2) THEN
31                  count := count + 1;
32                  IF (count=T) THEN
33                      count := 0;
34                      pr_state <= nx_state;
35                  END IF;
36              ELSE
37                  count := 0;
38              END IF;
39          END IF;
40      END PROCESS;
41      ----Upper section of FSM:-----
42      PROCESS (pr_state, x)
43      BEGIN
44          CASE pr_state IS
45              WHEN A =>
46                  y <= '1';
47                  T <= 1;
48                  input1<=0; input2<=1;
49                  nx_state <= B;
50              WHEN B =>
51                  y <= '0';
52                  T <= time1;
53                  input1<=2; input2<=2;
54                  nx_state <= C;
55              WHEN C =>
56                  y <= '1';
57                  T <= time2;
58                  input1<=3; input2<=3;
59                  nx_state <= A;
60          END CASE;
61      END PROCESS;
62  END ARCHITECTURE;
63  -----

```

 The view produced by the state machine viewer (with the *enum_encoding* attribute commented out) is shown below.



Timing diagram showing signals over 720 ns. The signals are: rst, clk, x, count, pr_state, and y. The diagram illustrates the sequence of events during the test, including the reset of the counter and the state transitions of the priority encoder.

A VHDL code for this problem is presented below. The code for the up/down counter, with 0.5 seconds in each state, is shown explicitly, while the parts already seen in examples in the book are just indicated. The clock frequency (entered as a generic parameter) was assumed to be 50 MHz. (Suggestion: See first the design in section 12.2.)

```

1  -----Package with function:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  PACKAGE my_functions IS
5      FUNCTION integer_to_lcd (SIGNAL input: NATURAL) RETURN STD_LOGIC_VECTOR;
6      ... (insert function integer_to_lcd seen in sec. 12.2)
7  END my_functions;
8  -----
9
10 -----Main code:-----
11 LIBRARY ieee;
12 USE ieee.std_logic_1164.all;
13 USE work.my_functions.all;
14 -----
15 ENTITY counter_with_LCD IS
16     GENERIC (
17         fclk: POSITIVE := 50_000_000;      --clock frequency (50MHz)
18         clk_divider: POSITIVE := 50_000);  --for LCD clock (500Hz)
19     PORT (
20         clk, rst, up: IN STD_LOGIC;
21         RS, RW, LCD_ON, BKL_ON: OUT STD_LOGIC;
22         E: BUFFER STD_LOGIC;
23         DB: OUT STD_LOGIC_VECTOR(7 DOWNTO 0));
24 END ENTITY;
25 -----
26 ARCHITECTURE counter_with_LCD OF counter_with_LCD IS
27     TYPE state IS (FunctionSet1, FunctionSet2, FunctionSet3, FunctionSet4,
28         ClearDisplay, DisplayControl, EntryMode, WriteData, ReturnHome);
29     SIGNAL pr_state, nx_state: state;
30     SIGNAL counter_output: NATURAL RANGE 0 TO 15;
31     SIGNAL lcd_input: STD_LOGIC_VECTOR(7 DOWNTO 0);
32 BEGIN
33     -----Counter (up/down, 0.5s per state):-----
34     PROCESS (clk, rst, up)
35         VARIABLE counter1: INTEGER RANGE 0 TO fclk/2;
36         VARIABLE counter2: INTEGER RANGE 0 TO 15;
37     BEGIN
38         IF (rst='1') THEN
39             counter1 := 0;
40             IF (up='1') THEN counter2 := 0;
41             ELSE counter2 := 15;
42             END IF;
43         ELSIF (clk'EVENT AND clk='1') THEN
44             IF (up='1') THEN
45                 IF (counter2 /= 15) THEN
46                     counter1 := counter1 + 1;
47                     IF (counter1=fclk/2) THEN

```



```

39         counter1 := 0;
40         counter2 := counter2 + 1;
41     END IF;
42 END IF;
43 ELSE
44     IF (counter2 /= 0) THEN
45         counter1 := counter1 + 1;
46         IF (counter1=fclk/2) THEN
47             counter1 := 0;
48             counter2 := counter2 - 1;
49         END IF;
50     END IF;
51 END IF;
52 END IF;
53 counter_output <= counter2;
54 END PROCESS;
55 -----LCD driver [Pedroni 2008]:-----
56 lcd_input <= integer_to_lcd(counter_output);
57 LCD_ON <= '1'; BKL_ON <= '1';
58 PROCESS (clk)
59     ... (insert code for LCD driver seen in sec. 12.2)
60 END PROCESS;
61 END ARCHITECTURE;
62 -----

```

Exercise 12.13: Frequency meter with Gray counter

The subject of this exercise is the very interesting and important issue of *clock domain crossing*. Only a brief visit to the subject is presented here, with the help of the figure below.

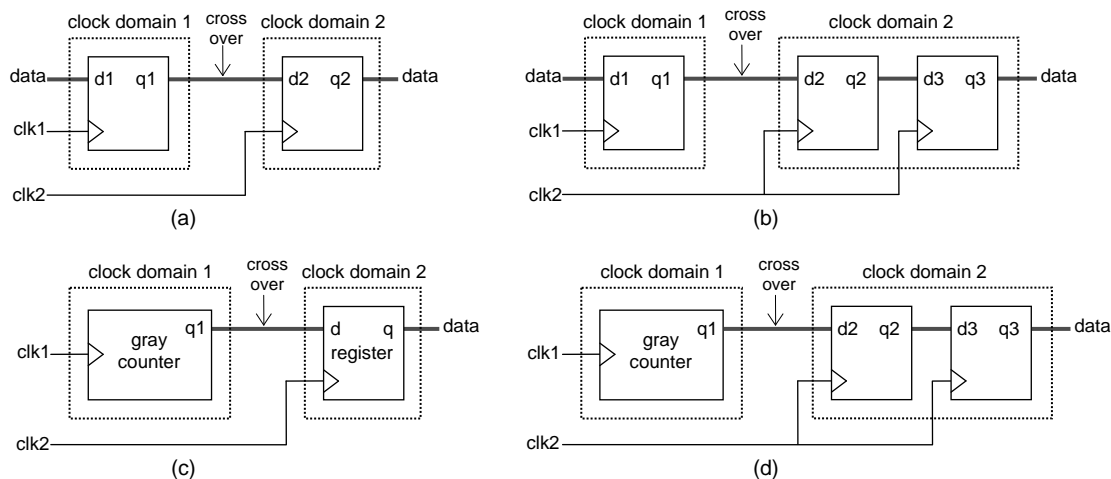


Figure (a) shows two interconnected domains. They operate with distinct (asynchronous with respect to each other) clocks, called *clk1* and *clk2*. The problem is that a positive edge in *clk2* can occur while the output of DFF1 (*q1*) is changing its value; in such a case, because the setup/hold times of DFF2 are not respected, a metastable state (a state between '0' and '1', which normally takes a relatively long time to settle) can occur at the output of DFF2.

The most popular synchronizer for clock domain crossing is depicted in figure (b), consisting simply of two-stage shift register, which causes the data signal (*data*) to be received without metastable states downstream. Another alternative is depicted in (c), which is adequate for the case when *data* is the output of a *counter*. Because in a gray counter [Pedroni 2008] only one bit changes at a time, if *clk2* activates the register while it is changing its value (that is, when this change occurs during the setup + hold times of the register), at most one bit will be stored with incorrect value, so the output cannot be more than one unit off the actual value. This, however, does not prevent the register from producing a metastable state, which can be cleaned using the same arrangement of figure (b), resulting the combined implementation of figure (d).

In terms of hardware usage, the solution with a synchronizer (figure (b)) requires two extra registers, with *N* flip-flops each (*N* is the number of bits in *data*), while the solution with just a gray counter (figure (c)) does not require additional flip-


flops, but does require additional combinational logic, consisting of a layer with $N-1$ XOR gates. Obviously, the solution in figure (d) requires the sum of both.

A straightforward implementation for a gray counter is to implement a regular sequential counter then convert its output to gray code using the equations below, where b is the output from the binary counter and g is the corresponding gray representation:

$$g(N-1) = b(N-1)$$

$$g(i) = b(i) \oplus b(i+1) \text{ for } i = 0, 1, \dots, N-2$$

A corresponding circuit is shown in the figure below, for $N=4$.

 

Exercise 13.5: ROM implemented with a HEX file #1

The only changes needed in the code of section 13.4, which employed CONSTANT to implement the ROM, are in the architecture declarations, replacing the original text with that below:

```
ARCHITECTURE rom OF rom_with_hex_file IS
    SIGNAL reg_address: INTEGER RANGE 0 TO 15;
    TYPE memory IS ARRAY (0 TO 15) OF STD_LOGIC_VECTOR(7 DOWNTO 0);
    SIGNAL myrom: memory;
    ATTRIBUTE ram_init_file: STRING;
    ATTRIBUTE ram_init_file OF myrom: SIGNAL IS "rom_contents.hex";
BEGIN
```

Remember to create a plain text file with the contents below (see the construction of MIF files in section 13.3), saved with the name *rom_contents.hex* in the work directory:

```
: 10 0000 00 00 00 FF 1A 05 50 B0 00 00 00 00 00 00 00 11 C1
: 00 0000 01 FF
```

Exercise 13.9: Synchronous RAM

See code for *memory3* in section 20.6 of [Pedroni 2008].

Exercise 14.10: I²C interface for an RTC

Note: Before examining this solution, please read the topic “Additional Details on the I²C Interface” in the “Extra Material” part of the book website.

PCF8563, PCF8573, PCF8583, and PCF8593 are part of the NXP family of RTC (real time clock) devices. For availability reasons, the RTC employed in this solution was PFC8593, which is an RTC with clock/calendar plus timer/alarm options. The clock/calendar features were explored in this design, which are set using the first eight memory bytes, shown in figure 1.

Figure 1. First eight bytes of the PCF8593 register.

```

1  ----Package with a function:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  PACKAGE my_functions IS
5      FUNCTION bin_to_ssd (CONSTANT input: STD_LOGIC_VECTOR) RETURN STD_LOGIC_VECTOR;
6  END my_functions;
7  -----
8  PACKAGE BODY my_functions IS
9      FUNCTION bin_to_ssd (CONSTANT input: STD_LOGIC_VECTOR) RETURN STD_LOGIC_VECTOR IS
10         VARIABLE output: STD_LOGIC_VECTOR(6 DOWNTO 0);
11     BEGIN
12         CASE input IS
13             WHEN "0000" => output:="0000001";          --"0" on SSD
14             WHEN "0001" => output:="1001111";          --"1" on SSD

```

```

15     WHEN "0010" => output:="0010010";      --"2" on SSD
16     WHEN "0011" => output:="0000110";      --"3" on SSD
17     WHEN "0100" => output:="1001100";      --"4" on SSD
18     WHEN "0101" => output:="0100100";      --"5" on SSD
19     WHEN "0110" => output:="0100000";      --"6" on SSD
20     WHEN "0111" => output:="0001111";      --"7" on SSD
21     WHEN "1000" => output:="0000000";      --"8" on SSD
22     WHEN "1001" => output:="0000100";      --"9" on SSD
23     WHEN "1010" => output:="0001000";      --"A" on SSD
24     WHEN "1011" => output:="1100000";      --"b" on SSD
25     WHEN "1100" => output:="0110001";      --"C" on SSD
26     WHEN "1101" => output:="1000010";      --"d" on SSD
27     WHEN "1110" => output:="0110000";      --"E" on SSD
28     WHEN OTHERS => output:="0111000";      --"F" on SSD
29     END CASE;
30     RETURN output;
31     END bin_to_ssd;
32 END PACKAGE BODY;
33 -----

1  ----Main code:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  USE work.my_functions.all; --package with "integer_to_ssd" function.
5  -----
6  ENTITY rtc_i2c IS
7      GENERIC (
8          --System parameters:
9          fclk: POSITIVE := 50_000; --Freq. of system clock (in kHz)
10         data_rate: POSITIVE := 100; --Desired I2C bus speed (in kbps)
11         slave_addr_for_write: STD_LOGIC_VECTOR(7 DOWNTO 0) := "10100010";
12         slave_addr_for_read: STD_LOGIC_VECTOR(7 DOWNTO 0) := "10100011";
13         initial_address_wr: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000";
14         initial_address_rd: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000010";
15         --Values to store in the RTC memory (clock/calendar settings):
16         set_control: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000";
17         set_subsec: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000"; --0.00 sec
18         set_sec: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000"; --00 sec
19         set_min: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00110000"; --30 min
20         set_hour: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00010100"; --14 h
21         set_date: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000001"; --01 day
22         set_month: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00010001"; --11 November
23         set_timer: STD_LOGIC_VECTOR(7 DOWNTO 0) := "00000000");
24  PORT (
25      --Clock and control signals:
26      clk, rst, wr, rd: IN STD_LOGIC;
27      --I2C signals:
28      SCL: OUT STD_LOGIC;
29      SDA: INOUT STD_LOGIC;
30      --System outputs (to SSD displays):
31      chip_rst: OUT STD_LOGIC;
32      ssd_sec: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --units of seconds
33      ssd_10sec: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --tens of seconds
34      ssd_min: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --units of minutes
35      ssd_10min: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --tens of minutes
36      ssd_hour: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --units of hours
37      ssd_10hour: OUT STD_LOGIC_VECTOR(6 DOWNTO 0); --tens of hours
38      ack_error: OUT STD_LOGIC); --to an LED
39  END ENTITY;
40  -----
41  ARCHITECTURE fsm OF rtc_i2c IS
42      --General signals:
43      CONSTANT divider: INTEGER := (fclk/8)/data_rate;
44      SIGNAL timer: NATURAL RANGE 0 TO 8;
45      SIGNAL aux_clk, bus_clk, data_clk: STD_LOGIC;
46      SIGNAL wr_flag, rd_flag: STD_LOGIC;
47      SIGNAL sec: STD_LOGIC_VECTOR(7 DOWNTO 0);
48      SIGNAL min: STD_LOGIC_VECTOR(7 DOWNTO 0);
49      SIGNAL hour: STD_LOGIC_VECTOR(7 DOWNTO 0);
50      SHARED VARIABLE i: NATURAL RANGE 0 TO 7 := 0;
51      --State-machine signals:
52      TYPE state IS (
53          --Common write+read states:
54          idle, start_wr, slave_addr_wr, ack1, stop,
55          --Write-only states:
56          initial_addr_wr, ack2, wr_control, ack3, wr_subsec, ack4, wr_sec, ack5, wr_min, ack6,
57          wr_hour, ack7, wr_date, ack8, wr_month, ack9, wr_timer, ack10,

```

```

58      --Read-only states:
59      initial_addr_rd, ack11, start_rd, slave_addr_rd, ack12, rd_sec, ack13, rd_min, ack14,
60      rd_hour, no_ack);
61      SIGNAL pr_state, nx_state: state;
62  BEGIN
63      chip_rst <= NOT rst; --to reset the chip (pin 3)
64      -----Display signals:-----
65      ssd_sec <= bin_to_ssd(sec(3 DOWNTO 0));
66      ssd_10sec <= bin_to_ssd(sec(7 DOWNTO 4));
67      ssd_min <= bin_to_ssd(min(3 DOWNTO 0));
68      ssd_10min <= bin_to_ssd(min(7 DOWNTO 4));
69      ssd_hour <= bin_to_ssd(hour(3 DOWNTO 0));
70      ssd_10hour <= bin_to_ssd("00" & hour(5 DOWNTO 4));
71      -----Auxiliary clock (400kHz):-----
72      PROCESS (clk)
73          VARIABLE count1: INTEGER RANGE 0 TO divider;
74      BEGIN
75          IF (clk'EVENT AND clk='1') THEN
76              count1 := count1 + 1;
77              IF (count1=divider) THEN
78                  aux_clk <= NOT aux_clk;
79                  count1 := 0;
80              END IF;
81          END IF;
82      END PROCESS;
83      -----Bus & data clocks (100kHz):-----
84      PROCESS (aux_clk)
85          VARIABLE count2: NATURAL RANGE 0 TO 3;
86      BEGIN
87          IF (aux_clk'EVENT AND aux_clk='1') THEN
88              count2 := count2 + 1;
89              IF (count2=0) THEN
90                  bus_clk <= '0';
91              ELSIF (count2=1) THEN
92                  data_clk <= '1';
93              ELSIF (count2=2) THEN
94                  bus_clk <= '1';
95              ELSE
96                  data_clk <= '0';
97              END IF;
98          END IF;
99      END PROCESS;
100     -----Lower section of FSM:-----
101     PROCESS (rst, data_clk)
102         VARIABLE error_flag: STD_LOGIC;
103     BEGIN
104         IF (rst='1') THEN
105             pr_state <= idle;
106             wr_flag <= '0';
107             rd_flag <= '0';
108             error_flag := '0';
109             i := 0;
110             --Enter data for I2C bus:
111             ELSIF (data_clk'EVENT AND data_clk='1') THEN
112                 IF (i=timer-1) THEN
113                     pr_state <= nx_state;
114                     i := 0;
115                 ELSE
116                     i := i + 1;
117                 END IF;
118             ELSIF (data_clk'EVENT AND data_clk='0') THEN
119                 --Store data read from RTC memory:
120                 IF (pr_state=rd_sec) THEN
121                     sec(7-i) <= SDA;
122                 ELSIF (pr_state=rd_min) THEN
123                     min(7-i) <= SDA;
124                 ELSIF (pr_state=rd_hour) THEN
125                     hour(7-i) <= SDA;
126                 END IF;
127                 --Store write/read/error flags:
128                 IF (pr_state=idle) THEN
129                     wr_flag <= wr;
130                     rd_flag <= rd;
131                 ELSIF (pr_state=stop) THEN
132                     wr_flag <= '0';
133                     rd_flag <= '0';
134                 ELSIF (pr_state=ack1 OR pr_state=ack2 OR pr_state=ack3 OR pr_state=ack4 OR
135                     pr_state=ack5 OR pr_state=ack6 OR pr_state=ack7 OR pr_state=ack8 OR pr_state=ack9

```

```

136         OR pr_state=ack10) THEN
137             error_flag := error_flag OR SDA;
138         END IF;
139     END IF;
140     ack_error <= error_flag;
141 END PROCESS;
142 -----Upper section of FSM:-----
143 PROCESS (pr_state, bus_clk, data_clk, wr_flag, rd_flag)
144 BEGIN
145     CASE pr_state IS
146         --common write-read states:
147         WHEN idle =>
148             SCL <= '1';
149             SDA <= '1';
150             timer <= 1;
151             IF (wr_flag='1' OR rd_flag='1') THEN
152                 nx_state <= start_wr;
153             ELSE
154                 nx_state <= idle;
155             END IF;
156         WHEN start_wr =>
157             SCL <= '1';
158             SDA <= data_clk; --or '0'
159             timer <= 1;
160             nx_state <= slave_addr_wr;
161         WHEN slave_addr_wr =>
162             SCL <= bus_clk;
163             SDA <= slave_addr_for_write(7-i);
164             timer <= 8;
165             nx_state <= ack1;
166         WHEN ack1 =>
167             SCL <= bus_clk;
168             SDA <= 'Z';
169             timer <= 1;
170             IF (wr_flag='1') THEN
171                 nx_state <= initial_addr_wr;
172             ELSE
173                 nx_state <= initial_addr_rd;
174             END IF;
175         --data-write states:
176         WHEN initial_addr_wr =>
177             SCL <= bus_clk;
178             SDA <= initial_address_wr(7-i);
179             timer <= 8;
180             nx_state <= ack2;
181         WHEN ack2 =>
182             SCL <= bus_clk;
183             SDA <= 'Z';
184             timer <= 1;
185             nx_state <= wr_control;
186         WHEN wr_control =>
187             SCL <= bus_clk;
188             SDA <= set_control(7-i);
189             timer <= 8;
190             nx_state <= ack3;
191         WHEN ack3 =>
192             SCL <= bus_clk;
193             SDA <= 'Z';
194             timer <= 1;
195             nx_state <= wr_subsec;
196         WHEN wr_subsec =>
197             SCL <= bus_clk;
198             SDA <= set_subsec(7-i);
199             timer <= 8;
200             nx_state <= ack4;
201         WHEN ack4 =>
202             SCL <= bus_clk;
203             SDA <= 'Z';
204             timer <= 1;
205             nx_state <= wr_sec;
206         WHEN wr_sec =>
207             SCL <= bus_clk;
208             SDA <= set_sec(7-i);
209             timer <= 8;
210             nx_state <= ack5;
211         WHEN ack5 =>
212             SCL <= bus_clk;
213             SDA <= 'Z';

```

```

214         timer <= 1;
215         nx_state <= wr_min;
216     WHEN wr_min =>
217         SCL <= bus_clk;
218         SDA <= set_min(7-i);
219         timer <= 8;
220         nx_state <= ack6;
221     WHEN ack6 =>
222         SCL <= bus_clk;
223         SDA <= 'Z';
224         timer <= 1;
225         nx_state <= wr_hour;
226     WHEN wr_hour =>
227         SCL <= bus_clk;
228         SDA <= set_hour(7-i);
229         timer <= 8;
230         nx_state <= ack7;
231     WHEN ack7 =>
232         SCL <= bus_clk;
233         SDA <= 'Z';
234         timer <= 1;
235         nx_state <= wr_date;
236     WHEN wr_date =>
237         SCL <= bus_clk;
238         SDA <= set_date(7-i);
239         timer <= 8;
240         nx_state <= ack8;
241     WHEN ack8 =>
242         SCL <= bus_clk;
243         SDA <= 'Z';
244         timer <= 1;
245         nx_state <= wr_month;
246     WHEN wr_month =>
247         SCL <= bus_clk;
248         SDA <= set_month(7-i);
249         timer <= 8;
250         nx_state <= ack9;
251     WHEN ack9 =>
252         SCL <= bus_clk;
253         SDA <= 'Z';
254         timer <= 1;
255         nx_state <= wr_timer;
256     WHEN wr_timer =>
257         SCL <= bus_clk;
258         SDA <= set_timer(7-i);
259         timer <= 8;
260         nx_state <= ack10;
261     WHEN ack10 =>
262         SCL <= bus_clk;
263         SDA <= 'Z';
264         timer <= 1;
265         nx_state <= stop;
266     --data-read states:
267     WHEN initial_addr_rd =>
268         SCL <= bus_clk;
269         SDA <= initial_address_rd(7-i);
270         timer <= 8;
271         nx_state <= ack11;
272     WHEN ack11 =>
273         SCL <= bus_clk;
274         SDA <= 'Z';
275         timer <= 1;
276         nx_state <= start_rd;
277     WHEN start_rd =>
278         SCL <= '1'; --or bus_clk;
279         SDA <= data_clk;
280         timer <= 1;
281         nx_state <= slave_addr_rd;
282     WHEN slave_addr_rd =>
283         SCL <= bus_clk;
284         SDA <= slave_addr_for_read(7-i);
285         timer <= 8;
286         nx_state <= ack12;
287     WHEN ack12 =>
288         SCL <= bus_clk;
289         SDA <= 'Z';
290         timer <= 1;
291         nx_state <= rd_sec;

```

```

292     WHEN rd_sec =>
293         SCL <= bus_clk;
294         SDA <= 'Z';
295         timer <= 8;
296         nx_state <= ack13;
297     WHEN ack13 =>
298         SCL <= bus_clk;
299         SDA <= '0';
300         timer <= 1;
301         nx_state <= rd_min;
302     WHEN rd_min =>
303         SCL <= bus_clk;
304         SDA <= 'Z';
305         timer <= 8;
306         nx_state <= ack14;
307     WHEN ack14 =>
308         SCL <= bus_clk;
309         SDA <= '0';
310         timer <= 1;
311         nx_state <= rd_hour;
312     WHEN rd_hour =>
313         SCL <= bus_clk;
314         SDA <= 'Z';
315         timer <= 8;
316         nx_state <= no_ack;
317     WHEN no_ack =>
318         SCL <= bus_clk;
319         SDA <= '1';
320         timer <= 1;
321         nx_state <= stop;
322     --Common write-read state:
323     WHEN stop =>
324         SCL <= bus_clk;
325         SDA <= NOT data_clk; --or '0'
326         timer <= 1;
327         nx_state <= idle;
328     END CASE;
329 END PROCESS;
330 END ARCHITECTURE;
331 -----

```

Exercise 15.1: 800x600x75Hz SVGA interface

All that is needed is to replace the values of H_{pulse} , H_{BP} , H_{active} , H_{FP} , V_{pulse} , V_{BP} , V_{active} , and V_{FP} with those for the SVGA standard. Such values are listed in section 17.3 and are used in the design of section 17.4.

Exercise 15.2: Image generation with hardware #1 (banner)

A major advantage of breaking the video interfaces into standard and non-standard parts, as done in chapters 15-17, is that most of the design stays always the same, so once it has been understood, doing other designs becomes relatively simple. To solve the present exercise, we only need to replace the code for Part 2 (image generator, lines 81-115) in section 15.9 with a new PROCESS, for the new image, which can be easily written based on the solution to exercise 17.2 shown ahead.

Exercise 15.3: Image generation with hardware #2 (sun in the sky)

As mentioned above, a major advantage of breaking the video interfaces into standard and non-standard parts, as done in chapters 15-17, is that most of the design stays always the same. To solve the present exercise, we only need to replace the code for Part 2 (image generator) in section 15.9 with a new code, for the new image, because the rest (control signals) remain the same. A code that solves this exercise is shown below (just replace lines 78-115 of the code in section 15.9 with this code).

```

1  -----
2  --Part 2: IMAGE GENERATOR
3  -----
4  PROCESS (pixel_clk, Hsync, dena)

```



```

5      VARIABLE x: NATURAL RANGE 0 TO Hd;
6      VARIABLE y: NATURAL RANGE 0 TO Vd;
7  BEGIN
8      ----Count columns:-----
9      IF (pixel_clk'EVENT AND pixel_clk='1') THEN
10         IF (Hactive='1') THEN x := x + 1;
11         ELSE x := 0;
12         END IF;
13     END IF;
14     ----Count lines:-----
15     IF (Hsync'EVENT AND Hsync='1') THEN
16         IF (Vactive='1') THEN y := y + 1;
17         ELSE y := 0;
18         END IF;
19     END IF;
20     --Generate the image:-----
21     IF (dena='1') THEN
22         IF ((x-320)**2+(y-240)**2)<14400) THEN
23             R <= (OTHERS => '1');
24             G <= (OTHERS => '1');
25             B <= (OTHERS => '0');
26         ELSE
27             R <= (OTHERS => red_switch);
28             G <= (OTHERS => green_switch);
29             B <= (OTHERS => blue_switch);
30         END IF;
31     ELSE
32         R <= (OTHERS => '0');
33         G <= (OTHERS => '0');
34         B <= (OTHERS => '0');
35     END IF;
36 END PROCESS;
37 -----

```

Exercise 15.4: Image generation with hardware #3 (filling with green)

As mentioned above, only the non-standard part of the VGA interface needs to be replaced. Take the code of section 15.9 and replace the code for Part 2 (image generator, lines 81-115) with a new PROCESS, for the new image, which can be easily written based on the solution to exercise 17.4, shown ahead.

Exercise 15.6: Image generation with hardware #5 (digital clock)

Again, the same code used in section 15.9 can be employed. Just replace Part 2 (image generator, lines 81-115) with a new code, for the new image, which can be based directly on the design presented in section 17.5. Note, however, that in the latter the image generator was constructed in two parts to ease its comprehension. Proper horizontal and vertical parameter adjustments might be needed, depending on the chosen display resolution.

Exercise 16.2: Image generation with hardware #1 (banner)

The same code used in section 16.7 can be employed here because it was already separated into standard and non-standard parts. The non-standard part (image generator) must be replaced with a code for the new image, while the other sections (control, serializer, etc.) remain the same. In summary, take the code of section 16.7 and replace its Part 1 (image generator) with a code similar to that shown in the solution to exercise 17.2, shown ahead. Make proper horizontal and vertical parameter adjustments according with the display resolution that you have chosen. Do not forget to create a file for the PLL (see sections 14.2 and 16.7).

Exercise 16.3: Image generation with hardware #2 (sun in the sky)

As mentioned above, the same code used in section 16.7 can be employed here because it was already separated into standard and non-standard parts. Take the code of section 16.7 and replace its Part 1 (image generator) with a code for the new image, which can be easily written based on the solution to exercise 17.3, shown ahead. Recall that the circle's

center must be at the center of the screen, so its coordinates must be adjusted according with the resolution chosen for the display. Do not forget to create a file for the PLL (see sections 14.2 and 16.7).


Exercise 16.4: Image generation with hardware #3 (filling with green)

Again, the same code used in section 16.7 can be employed. Just replace Part 1 (image generator) with a code for the new image, which can be easily written based on the solution to exercise 17.4, shown ahead. Make proper horizontal and vertical parameter adjustments according with the display resolution that you have chosen. Do not forget to create a file for the PLL (see sections 14.2 and 16.7).

Exercise 16.6: Image generation with hardware #5 (wall clock)

Again, the same code used in section 16.7 can be employed here because it was already separated into standard and non-standard parts. Only Part 1 (image generator) needs to be replaced. Since a wall clock was designed in section 17.5, that code can be used here. In summary, take the code of section 16.7 and replace its Part 1 with Part 1 and Part 2 of the wall clock (in section 17.5, the image generator was constructed in two parts to ease its comprehension). The only changes needed in the code brought from section 17.5 are adjustments in the horizontal and vertical parameters. Do not forget to create a file for the PLL (see sections 14.2 and 16.7).

 Exercise 17.2: Image generation with hardware C1 (banner)



As seen in the examples of chapters 15-17, a major advantage of separating the video interfaces in standard and non-standard parts is that most of them stay always the same. Thus the code of section 17.4 can be used here, replacing only Part 1 (image generator) with the code below. Obviously, because the image generator is instantiated in the main code, some adjustments might be needed in the declaration and instantiation of the image generator there. Recall also that the screen here is 600×800 pixels. Do not forget to create a file for the PLL (see sections 14.2 and 17.4).

```

1  -----Image generator:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY image_generator IS
6      PORT (
7          red_switch, green_switch, blue_switch: IN STD_LOGIC;
8          clk50, Hsync, Vsync, Hactive, Vactive, dena: IN STD_LOGIC;
9          R, G, B: OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
10 END image_generator;
11 -----
12 ARCHITECTURE image_generator OF image_generator IS
13 BEGIN
14     PROCESS (clk50, dena)
15         VARIABLE x: INTEGER RANGE 0 TO 800;
16         VARIABLE y: INTEGER RANGE 0 TO 600;
17     BEGIN
18         ----Count columns:-----
19         IF (clk50'EVENT AND clk50='1') THEN
20             IF (Hactive='1') THEN x := x + 1;
21             ELSE x := 0;
22             END IF;
23         END IF;
24         ----Count lines:-----
25         IF (Hsync'EVENT AND Hsync='1') THEN
26             IF (Vactive='1') THEN y := y + 1;

```

```


27         ELSE y := 0;
28         END IF;
29     END IF;
30     --Generate the image:-----
31     IF (dena='1') THEN
32         IF (x<700-y) THEN
33             R <= (OTHERS => red_switch);
34             G <= (OTHERS => green_switch);
35             B <= (OTHERS => blue_switch);
36         ELSE
37             R <= (OTHERS => NOT red_switch);
38             G <= (OTHERS => NOT green_switch);
39             B <= (OTHERS => NOT blue_switch);
40         END IF;
41     ELSE
42         R <= (OTHERS => '0');
43         G <= (OTHERS => '0');
44         B <= (OTHERS => '0');
45     END IF;
46     END PROCESS;
47 END image_generator;
48 -----

```

Exercise 17.3: Image generation with hardware #2 (sun in the sky)

As seen in the examples of chapters 15-17, a major advantage of separating the video interface in standard and non-standard parts is that most of them stay always the same. Thus the code of section 17.4 can be used here, replacing only Part 1 (image generator) with the code below. Obviously, because the image generator is instantiated in the main code, some adjustments might be needed in the declaration and instantiation of the image generator there. Recall that the screen size is 600×800 pixels and that the sun's radius must be 150 pixels (see the figure below). Do not forget to create a file for the PLL (see sections 14.2 and 17.4).

"Sun in the sky" (600×800)

 

```

1  -----Image generator:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY image_generator IS
6      PORT (
7          red_switch, green_switch, blue_switch: IN STD_LOGIC;
8          clk50, Hsync, Vsync, Hactive, Vactive, dena: IN STD_LOGIC;
9          R, G, B: OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
10 END image_generator;
11 -----
12 ARCHITECTURE image_generator OF image_generator IS
13 BEGIN
14     PROCESS (clk50, Hsync, dena)
15         VARIABLE x: INTEGER RANGE 0 TO 800;
16         VARIABLE y: INTEGER RANGE 0 TO 600;
17     BEGIN
18         --Count columns:-----
19         IF (clk50'EVENT AND clk50='1') THEN
20             IF (Hactive='1') THEN x := x + 1;
21             ELSE x := 0;
22         END IF;
23     END IF;
24     --Count lines:-----
25     IF (Hsync'EVENT AND Hsync='1') THEN
26         IF (Vactive='1') THEN y := y + 1;
27         ELSE y := 0;
28     END IF;
29     END IF;
30     --Generate the image:-----
31     IF (dena='1') THEN

```

```

32     IF ((x-400)**2+(y-300)**2)<22500) THEN
33         R <= (OTHERS => '1');
34         G <= (OTHERS => '1');
35         B <= (OTHERS => '0');
36     ELSE
37         R <= (OTHERS => red_switch);
38         G <= (OTHERS => green_switch);
39         B <= (OTHERS => blue_switch);
40     END IF;
41 ELSE
42     R <= (OTHERS => '0');
43     G <= (OTHERS => '0');
44     B <= (OTHERS => '0');
45 END IF;
46 END PROCESS;
47 END image_generator;
48 -----

```

Exercise 17.4: Image generation with hardware #3 (filling with green)

As mentioned above, a major advantage of separating the video interface in standard and non-standard parts is that most of them stay always the same. Thus the code of section 17.4 can be used here, replacing only Part 1 (image generator) with the code below. Do not forget to create a file for the PLL (see sections 14.2 and 17.4).

```

1  -----Image generator:-----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY image_generator IS
6      PORT (
7          red_switch, green_switch, blue_switch: IN STD_LOGIC;
8          Hsync, Vsync, Hactive, Vactive, dena: IN STD_LOGIC;
9          R, G, B: OUT STD_LOGIC_VECTOR(5 DOWNTO 0));
10 END image_generator;
11 -----
12 ARCHITECTURE image_generator OF image_generator IS
13 BEGIN
14     PROCESS (Hsync, Vsync, dena)
15         VARIABLE y: INTEGER RANGE 0 TO 600;
16         VARIABLE limit: INTEGER RANGE 0 TO 600;
17         VARIABLE flag: STD_LOGIC;
18     BEGIN
19         --Count lines:-----
20         IF (Hsync'EVENT AND Hsync='1') THEN
21             IF (Vactive='1') THEN
22                 y := y + 1;
23             ELSE
24                 y := 0;
25             END IF;
26         END IF;
27         --Generate vert. limit:-----
28         IF (Vsync'EVENT AND Vsync='1') THEN
29             limit := limit + 1;
30             IF (limit=600) THEN
31                 limit := 0;
32                 flag := NOT flag;
33             END IF;
34         END IF;
35         --Generate the image:-----
36         IF (dena='1') THEN
37             IF (flag='0') THEN
38                 IF (y<=limit) THEN
39                     R <= (OTHERS => '0');
40                     G <= (OTHERS => '1');
41                     B <= (OTHERS => '0');
42                 ELSE
43                     R <= (OTHERS => red_switch);
44                     G <= (OTHERS => green_switch);
45                     B <= (OTHERS => blue_switch);
46                 END IF;
47             ELSE
48                 IF (y>limit) THEN
49                     R <= (OTHERS => '0');
50                     G <= (OTHERS => '1');

```

```
51         B <= (OTHERS => '0');
52     ELSE
53         R <= (OTHERS => red_switch);
54         G <= (OTHERS => green_switch);
55         B <= (OTHERS => blue_switch);
56     END IF;
57 END IF;
58 ELSE
59     R <= (OTHERS => '0');
60     G <= (OTHERS => '0');
61     B <= (OTHERS => '0');
62 END IF;
63 END PROCESS;
64 END image_generator;
65 -----
```
